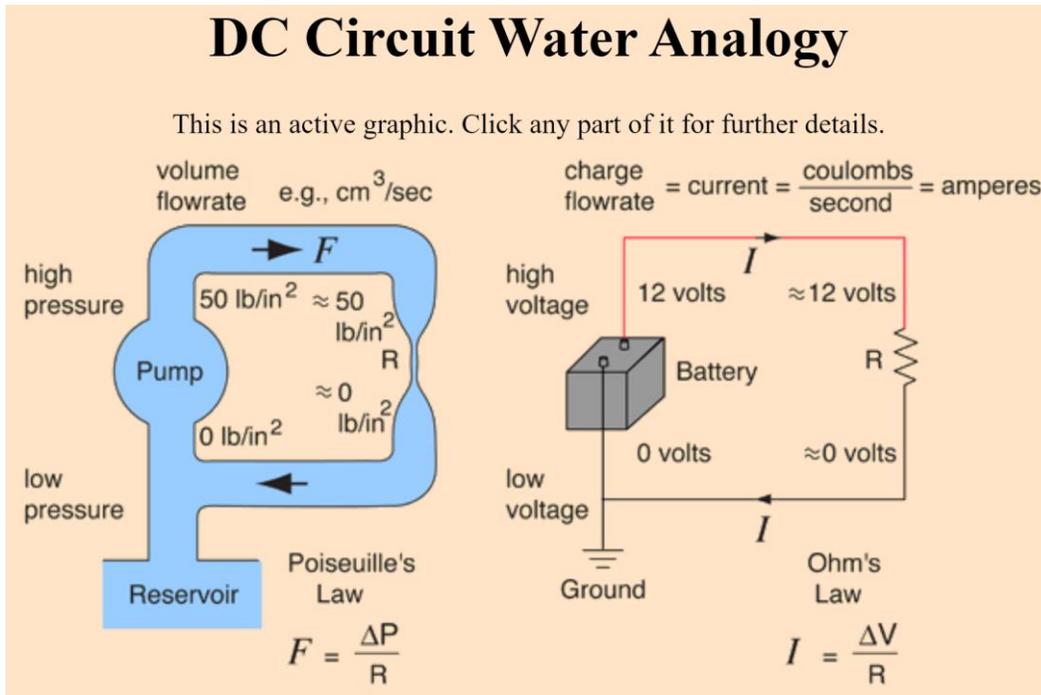


1. There are AC circuits and DC circuits. Right now we are focusing on DC electricity. What do AC and DC mean?
2. What is an electric circuit?



3. In the water circuit, above, what makes the water move?
4. In the electrical circuit, what makes the electricity move?
5. In the electrical circuit, what is the word that we use for the amount of charge that flows around the circuit?
6. In the water circuit, what slows down the water during its trip around the circuit?
7. What slows down the electrical current as it travels around the electrical circuit?

Playing with Circuits: pHet Simulation [Circuit Construction Kit: DC](#)

8. Build a simple circuit with one light bulb and one battery. Then find a way to cause **more** current to flow by adding another bulb to the circuit. Sketch what your final circuit looks like.

9. Build a simple circuit with one light bulb and one battery. Then find a way to cause **less** current to flow by adding another bulb to the circuit. Sketch what your final circuit looks like.

10. Find two ways to speed up current. Describe them here.

11. We say current flows from positive to negative. This sort of current is called “conventional current.” In reality, electrons move from negative to positive. Change the current mode from electron flow to conventional current and observe what happens. You don’t have to write anything here.

12. Use the voltmeter to measure the voltage of a battery. Do this by touching the probes to opposite ends of the battery. What is the voltage of one battery?

13. Use the ammeter to measure current. What unit is current measured in – what is it’s letter?

14. What causes fires to occur?

15. What other types of objects (other than wire) can you find that can be used to build circuits?

16. What is the purpose of the fuse? Find out and then explain here. If you want a hint, search it up on the internet.