

Physics 200 Unit 8 Handout, Part 2 Name: _____

Electric Current Again (some new stuff and some review)

1. Write the equation for electric current (and identify the symbols):

2. The unit of electric charge is the _____, which is equal in absolute magnitude to the charge of _____ electrons or protons.

3. 1 ampere = 1 "Amp" = 1A = 1 _____ /second.

4. If a cell phone is charging with a current of 0.5A, how many electrons are passing through its circuit each second?


5. By convention, the direction of current flow is from _____ to _____. The direction of conventional current is the direction that _____ charge would flow, if it did (but it doesn't -- in wires).

6. In metal wires, current is carried by _____. So it is _____ charges that are moving, and they are moving oppositely to conventional current.

7. The fact that conventional current is taken to be in the direction that positive charge would flow can be traced back to American politician and scientist _____. He named the type of charge associated with electrons

8. Electrical signals are known to move very rapidly. Most electrical signals carried by currents travel at speeds on the order of _____ m/s, a significant fraction of the speed of light. However, the actual electrons move much more slowly on average, typically drifting at speeds on the order of _____ m/s. This means it takes an electron in a wire about _____ seconds to travel one meter. Another example of sending messages quickly, across great distances, via a slowly-moving medium is provided by _____

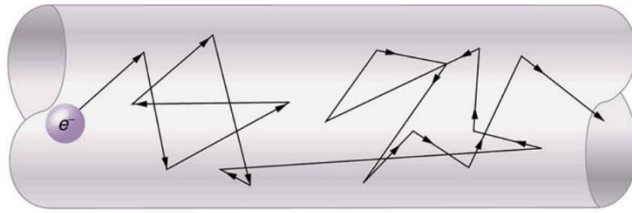9. Show the directions of the electron drift velocity v_d and the current I .



Resistances:

10. Resistances range over many orders of magnitude. Some ceramic insulators, such as those used to support power lines, have resistances of $10^{12} \Omega$ or more. A dry person may have a hand-to-foot resistance of $10^5 \Omega$, whereas the resistance of the human heart is about $10^3 \Omega$. A meter-long piece of large-diameter copper wire may have a resistance of _____, and superconductors have a resistance of _____.

Electric Power and Energy

11. Power (P) is the _____ of energy use or energy conversion.

12. Voltage (change in electric potential) can be expressed as J/C , and Current (Amperes) can be expressed as C/s .

$$J/C \times C/s = J/s. \text{ Therefore, } \underline{\hspace{2cm}} = P$$

13. The unit for power is the _____.

14. $1 \text{ W} = 1$ _____

15. Power companies charge their customers in units of kWh (kilowatt-hours). Kilowatt-hours isn't power. What is it? What's its equivalent in the units that we ordinarily use in this class?

16. Green Mountain Power presently charges about \$0.215 for each kWh. At that rate, how much would it cost to leave a 30W LED lightbulb on for 24 hours?

The Truth About Voltage

In a circuit, **Potential Energy** is the amount electric energy (Joules) stored in the charges - and delivered by them as they travel through the resistors. **Potential** (without the "energy") is the ratio of potential energy per unit of charge (Joules per Coulomb). If the potential is 3 J/C, and the current is 2A (2C/s), then 6J/s (6 Watts) of power is being consumed. Potential has the same units as Voltage (V).

Potential Difference (a.k.a. Voltage) is the change in potential between one part of the circuit and another. If the potential upstream from a resistor is 7V, and the potential downstream from the resistor is 3V, then the voltage across the resistor is -4V. This is often called the "voltage drop," even though it's redundant.

Another Circuit Analogy: Electric Circuits as Distribution Networks

<u>Amazon Distribution Network Component(s)</u>	<u>Electricity Analog</u>	<u>Symbols</u>	<u>Units</u>	<u>Source Units</u>
Packages	Energy	E	Joules (J)	
		Q	Coulombs (C)	
		V	Volts (V)	J/C
		I	Amperes (A)	C/s
		P	Watts (W)	J/s


Something the analogies/models don't explain - why do more powerful devices have less resistance?

Here's what works for me...

Imagine that each electrical device gets its energy from one or more tiny water wheels that turn as water flows by. Further imagine that each water wheel is fed by its own water pipe and that every pipe with its water wheel is identical to every other. A powerful device has more pipes for current to travel through. A low-power device has very few pipes - maybe just one. These pipes are essentially "holes" passing through the device (even though they have some resistance, due to the wheels). More holes passing through a device means water can flow through more easily, so there is less overall resistance. More holes/pipes also means more water wheels are getting turned, so the device gets more power.



Practice Analyzing A Circuit From an Energy Distribution Standpoint:

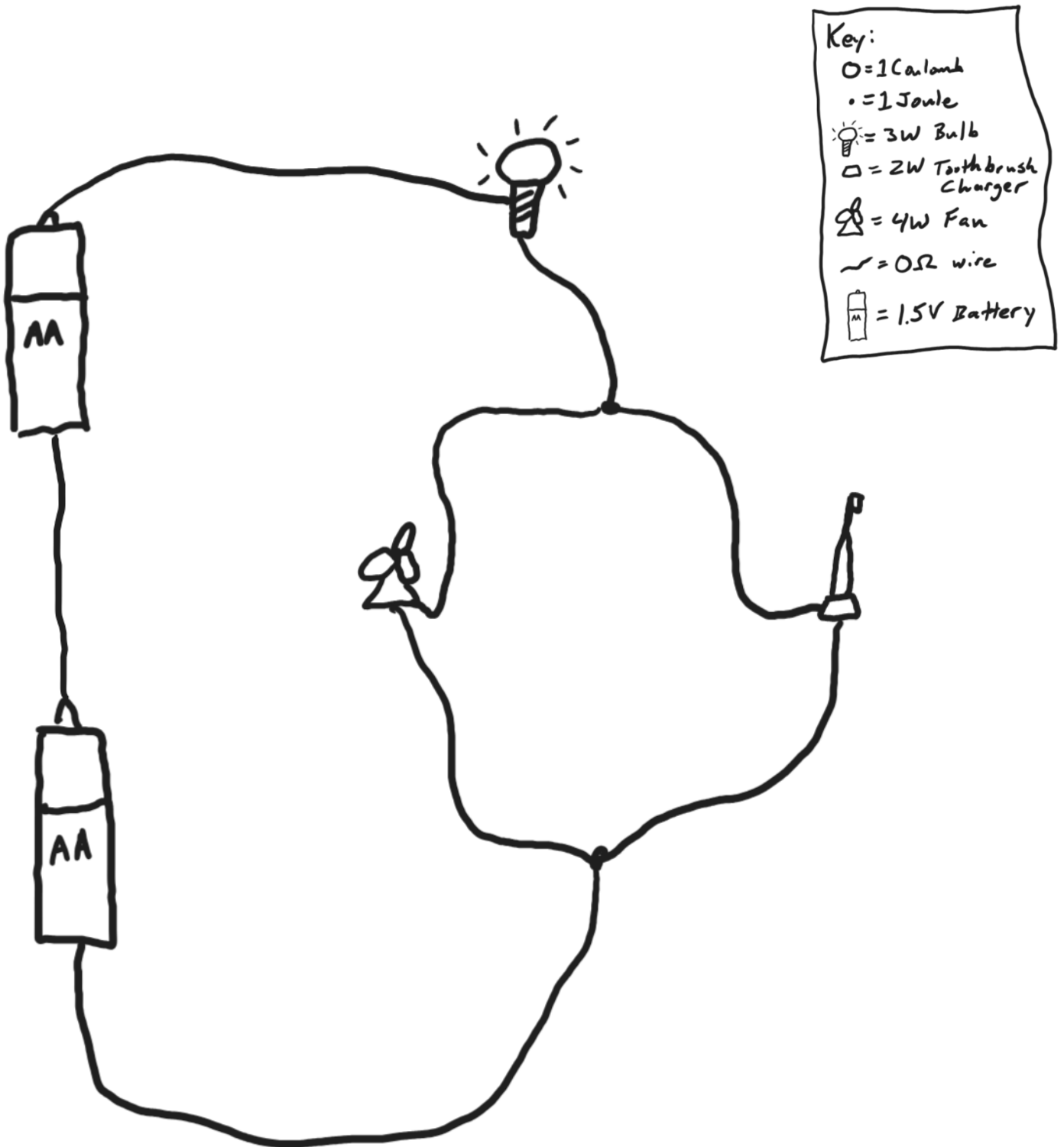- Illustrate/label potential, voltage, current, power, resistance, and energy in the circuit below. Use the information from the key.
- Show the charges passing through each wire segment during 1 second.



Practice: Someone is using a car battery to power a mini-amplifier and a wireless router. This is a little complicated because the two devices require 9V, but car batteries produce 12V. To solve the problem a resistor has been added, and the two devices are getting the power and voltage that they need.

- Illustrate/label potential, voltage, current, power, resistance, and energy in the circuit below. Use the information from the key.
- Note that, for this circuit, we are using one dot for 3J of energy, so you don't have to draw so many dots.
- Show the charges passing through each wire segment during 1 second.
- Don't make this at home! The resistor would get really hot!
- Start this one by first finding all of the resistances.

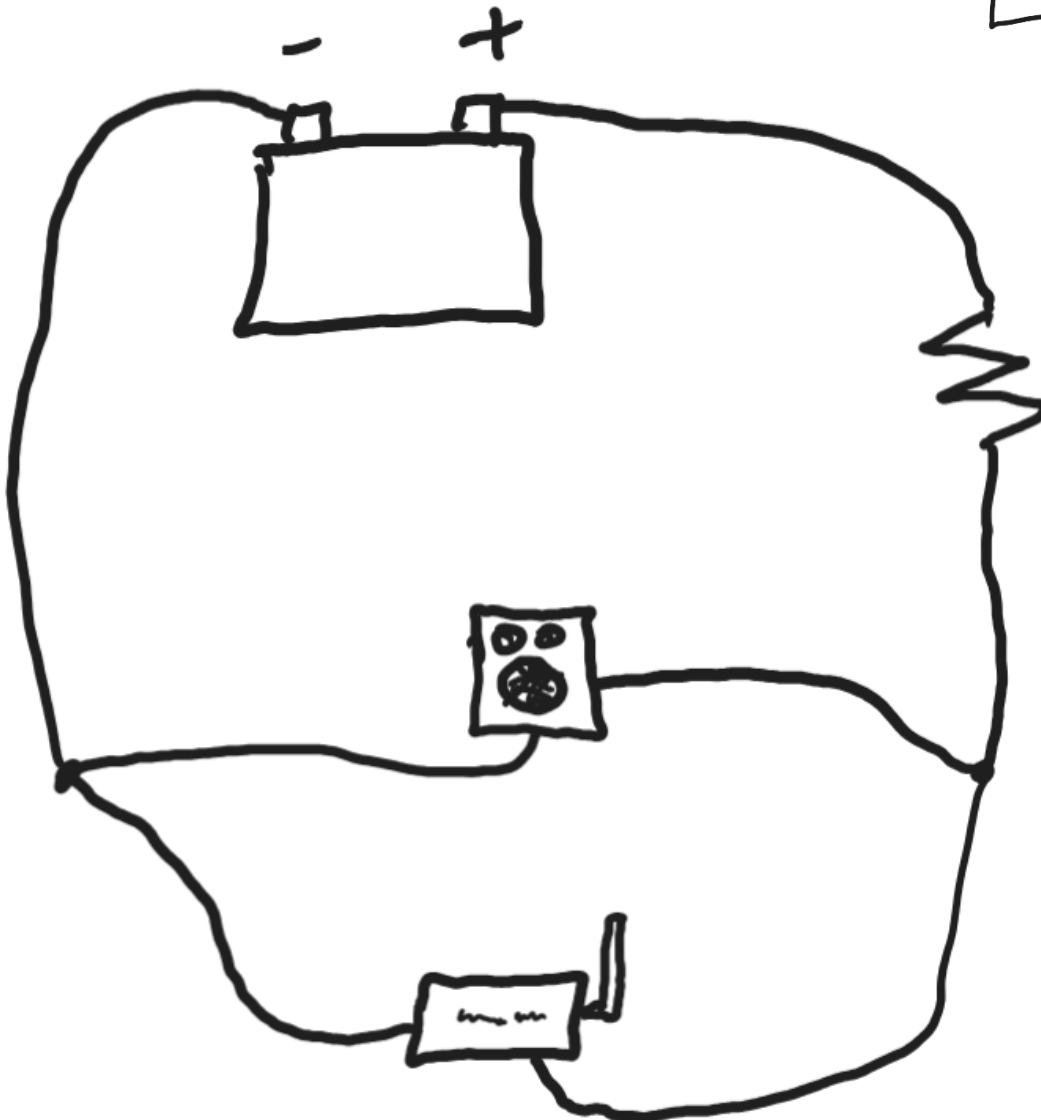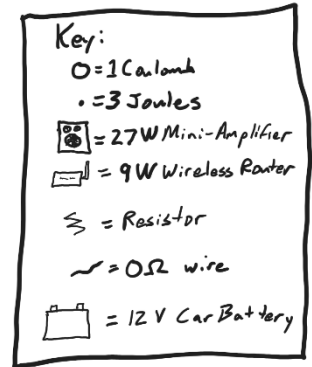

Circuit Reduction Practice – The Nine Companions


Use these formulas to find equivalent resistances of the following circuits:

$$R_{Tot\ Series} = R_1 + R_2 + R_3 \dots$$


$$\frac{1}{R_{Tot\ Parallel}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots$$

Assume each resistor has a value of 10 Ohms.


1.

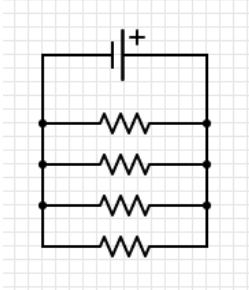


2.

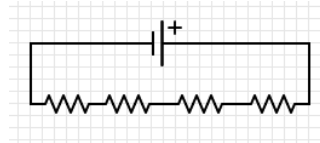


3.

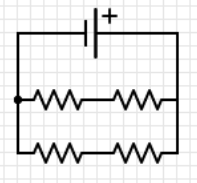


4.

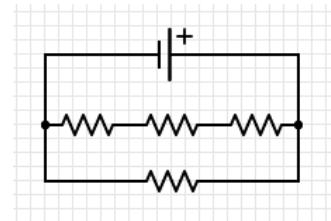


5.

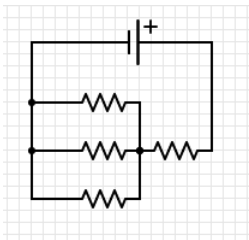


6.

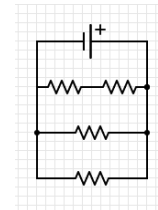


7.

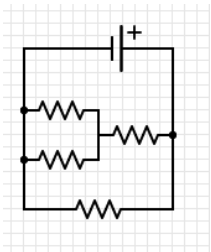

8.

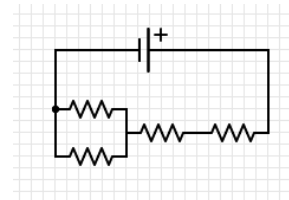

9.

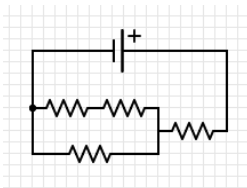

Answers:

1. 2.5 Ω

2. 40 Ω

3. 10 Ω

4. 7.5 Ω

5. 13.3 Ω


6. 4 Ω

7. 6 Ω


8. 25 Ω

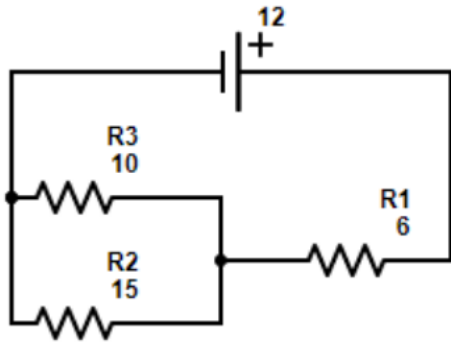9. 16.7 Ω


Circuit Practice: Find everything in the table.




	V	I	R	P
Source	12			
R ₁			6	
R ₂			15	
R ₃			10	

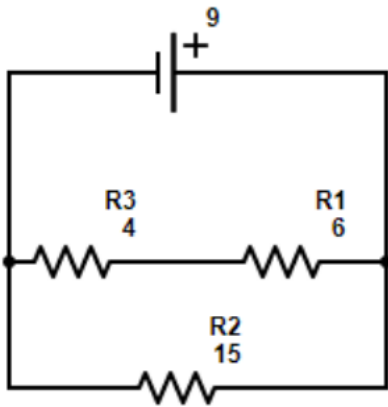

	V	I	R	P
Source	9			
R ₁			6	
R ₂			15	
R ₃			4	

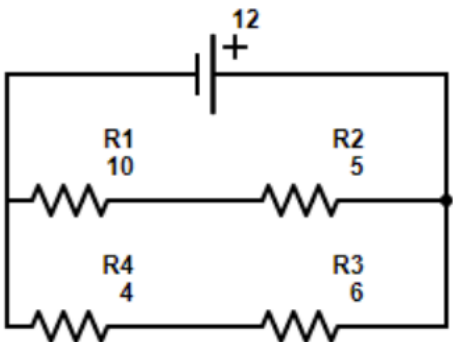


	V	I	R	P
Source	12			
R ₁			10	
R ₂			5	
R ₃			6	
R ₄			4	

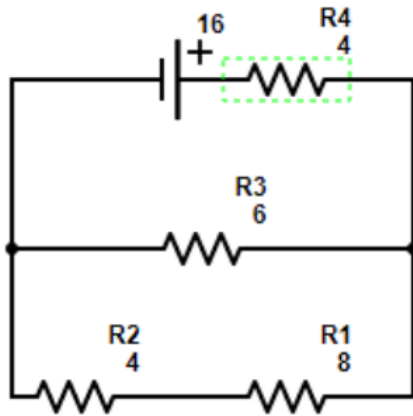

	V	I	R	P
Source	16			
R ₁			8	
R ₂			4	
R ₃			6	
R ₄			4	

S1 is Open

	V	I	R	P
Source	24			
R ₁			1	
R ₂			16	
R ₃			8	
R ₄			12	

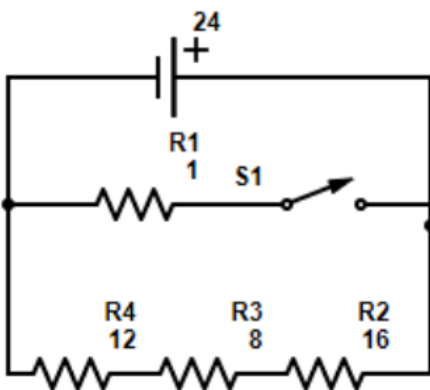

S1 is Closed

	V	I	R	P
Source	24			
R ₁			1	
R ₂			16	
R ₃			8	
R ₄			12	