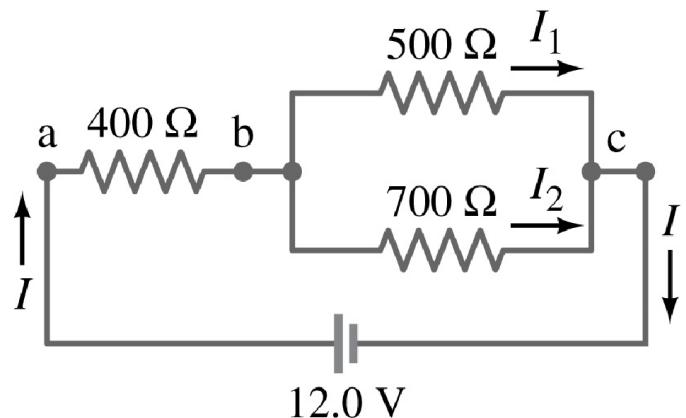


Name: \_\_\_\_\_

Physics 200 (Stapleton) Chapter 21 Equivalent Resistance Challenge

Problem 1

- A. Find the equivalent resistance of this circuit.



- B. Find the current passing through the battery.

- C. 400  $\Omega$  Resistor

- i. Find  $V$

- ii. Find  $I$

- iii. Find  $P$

- D. 500  $\Omega$  Resistor


- i. Find  $V$

- ii. Find  $I$

- iii. Find  $P$

Problem 2

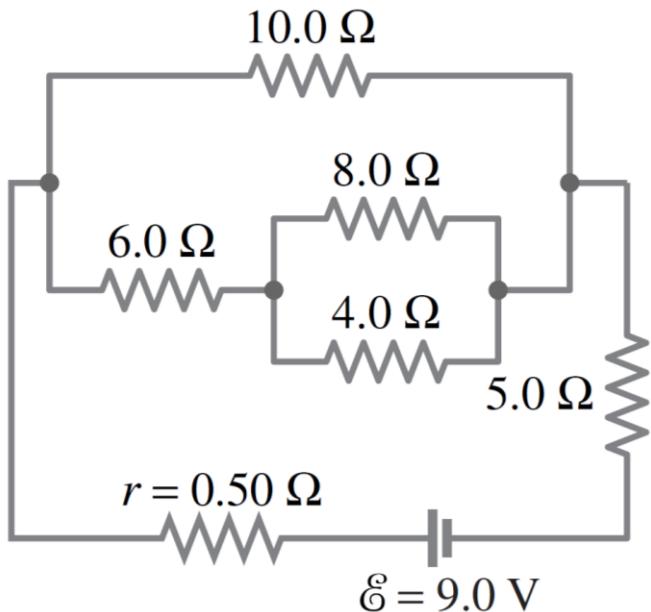A. Find the equivalent resistance of this circuit.



B. Find the current passing through the battery.

C.  $10.0 \Omega$  Resistor

i. Find  $V$

ii. Find  $I$

iii. Find  $P$

D.  $4.0 \Omega$  Resistor

i. Find  $V$

ii. Find  $I$

iii. Find  $P$

**Solutions:**

Prob 1: A.  $6.92 \Omega$     B.  $0.0173 \text{ A}$     C.i.  $6.94 \text{ V}$     ii.  $0.0173 \text{ A}$     iii.  $0.120 \text{ W}$     D.i.  $5.06 \text{ V}$     ii.  $0.0101 \text{ A}$     iii.  $0.0512 \text{ W}$

Prob 2: A.  $10.1 \Omega$     B.  $0.887 \text{ A}$     C.i.  $4.12 \text{ V}$     ii.  $0.412 \text{ A}$     iii.  $1.70 \text{ W}$     D.i.  $1.27 \text{ V}$     ii.  $0.317 \text{ A}$     iii.  $0.402 \text{ W}$