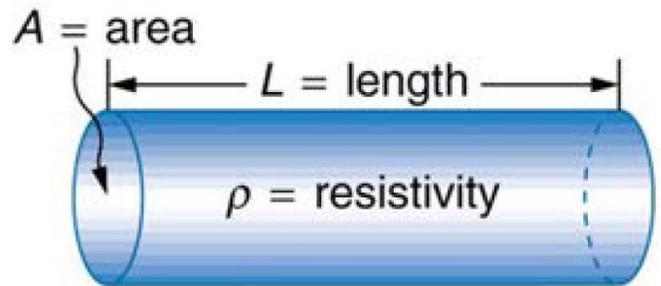


**Notes - 20.3 Resistance and Resistivity**

1. The resistance of an object depends on its \_\_\_\_\_ and the \_\_\_\_\_ of which it is composed.

2.  $R =$

3. Resistivity  $\rho$  is an \_\_\_\_\_ of the material, independent of its shape or size.



4. In home wiring, currents are limited and minimum wire thicknesses are specified because, as current and resistance increase, more \_\_\_\_\_ is produced in the wires,

4.5 Example Problem: What is the resistance of a 20.0-m-long piece of 12-gauge copper wire having a 2.053-mm diameter? ( $\rho_{Cu} = 1.72 \times 10^{-8} \Omega \cdot m$ )

**Notes - 20.4 Electric Power and Energy**

5. Power (P) is the \_\_\_\_\_ of energy use or energy conversion.

6. Voltage (electric potential) can be expressed as J/C, and Current (Amperes) can be expressed as C/s. Therefore,  $P =$  \_\_\_\_\_

7. The unit for power is \_\_\_\_\_.

8.  $1 \text{ W} = 1$  \_\_\_\_\_

9. Given that  $V = IR$ , alternate expressions for power include:


$P =$

10. Power companies do not charge for power, they charge for \_\_\_\_\_, which is sold to you in units called kilowatt-hours.  $1\text{kWh} = \text{_____J}$ .

**Notes - 21.1 Resistors in Series and Parallel**

11. Most circuits have more than one component, called a resistor that limits the flow of charge in the circuit. A measure of this limit on charge flow is called \_\_\_\_\_.

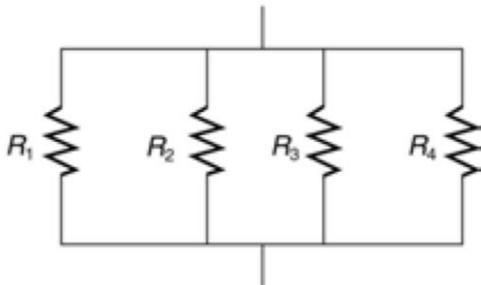12. Label which resistors are in series and which are in parallel.



\_\_\_\_\_



\_\_\_\_\_

13. **Resistors in Series:**

A. Series resistances add.  $R_{\text{series}} = \text{_____}$

B. The current flowing through resistors in series is

\_\_\_\_\_

C. Individual resistors \_\_\_\_\_ the overall voltage drop.

14. **Resistors in Parallel:**

A. Individual resistors' voltages \_\_\_\_\_

B. Resistors in parallel \_\_\_\_\_ the overall source current.

C. Parallel resistances are found from \_\_\_\_\_

15. Suppose the voltage output of a battery is 12.0 V, and the resistances for 3 resistors connected in **series** with the battery are  $R_1 = 1.00 \Omega$ ,  $R_2 = 6.00 \Omega$  and  $R_3 = 13.0 \Omega$ .
- Draw a diagram of the circuit.
  - What is the total resistance?
  - Find the current.
  - Calculate the voltage drop in each resistor, and show these add to equal the voltage output of the source.
  - Calculate the power dissipated by each resistor.
  - Find the power output of the source, and show that it equals the total power dissipated by the resistors.

