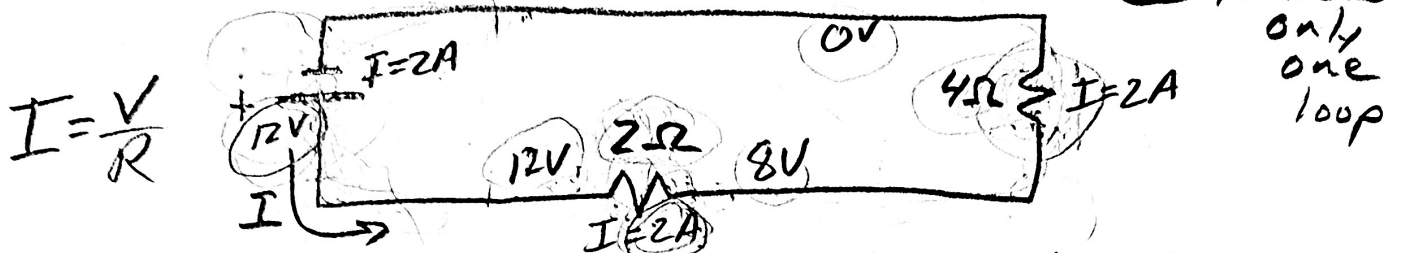



Notes - 21.1 Resistors in Series and Parallel

1. Suppose the voltage output of a battery is 12.0 V, and the resistances for 2 resistors connected in series with the battery are $R_1 = 2.00 \Omega$ and $R_2 = 4 \Omega$.

A. Draw a diagram of the circuit. What makes it a series circuit?



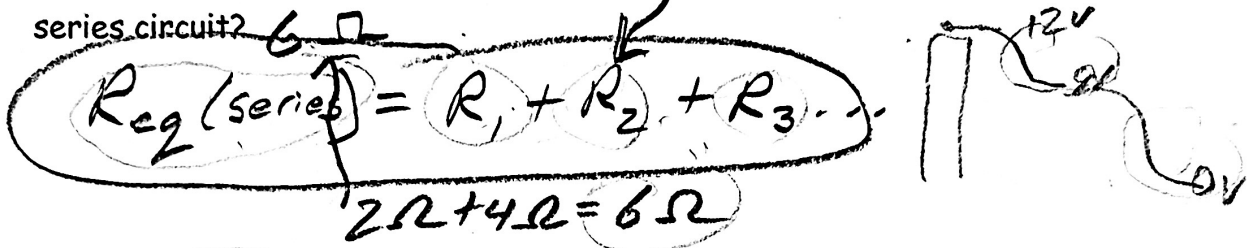B. What is the total resistance? What's the rule for equivalent resistance in a series circuit?



C. Find the current. What's the rule for individual and overall currents in a series circuit?

$I_{tot} = \frac{12V}{6\Omega} = 2A$

$I_{tot} = I_1 = I_2 = I_3 \dots$

D. Calculate the voltage drop in each resistor. What's the rule for individual and overall currents in a series circuit?

$V = IR$

$V_{2\Omega} = 2A(2\Omega) = 4V$

$V_{4\Omega} = 2A(4\Omega) = 8V$

$V_{Total} = 12V$

$V_{Total} = V_1 + V_2 + V_3 \dots$

E. Calculate the power dissipated by each resistor. What's the rule for power consumed by individual resistors, and overall, in a series circuit?

$P = IV$

$P_{2\Omega} = 2A(4V) = 8W$


$P_{4\Omega} = 2A(8V) = 16W$

$P_{Total} = P_1 + P_2 + P_3 \dots$

$P_{Total} = 2A(12V) = 24W$

16. Suppose the voltage output of a battery is 12.0 V, and the resistances for 2 resistors connected in parallel with the battery are $R_1 = 2.00 \Omega$ and $R_2 = 4 \Omega$.

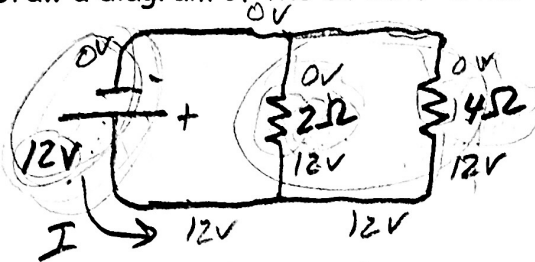A. Draw a diagram of the circuit. What makes it a parallel circuit?



multiple loops (paths) for charge to flow

B. What is the total resistance? What's the rule for equivalent resistance in a parallel circuit?

$$\frac{1}{R_{Tot}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots$$

$$\frac{1}{2\Omega} + \frac{1}{4\Omega} = \frac{1}{R_{Tot}}$$

$$\frac{3}{4\Omega} = \frac{1}{R_{Tot}} \quad R_{Tot} = \frac{4}{3}\Omega$$

C. Find the current. What's the rule for individual and overall currents in a parallel circuit?

$$I = \frac{V}{R}$$

$$I_{2\Omega} = \frac{12V}{2\Omega} = 6A$$

$$I_{4\Omega} = \frac{12V}{4\Omega} = 3A$$

$$I = \frac{12V}{\frac{4}{3}\Omega} = 9A$$

$$I_{Tot} = I_1 + I_2 + I_3 \dots$$

D. Calculate the voltage drop in each resistor. What's the rule for individual and overall currents in a parallel circuit?

$$V_{Tot} = V_1 = V_2 = V_3 \dots = 12V$$

E. Calculate the power dissipated by each resistor. What's the rule for power consumed by individual resistors, and overall, in a parallel circuit?

$$P = IV \quad P_{Tot} = P_1 + P_2 + P_3$$

$$P_{2\Omega} = 6A(12V) = 72W$$

$$P_{4\Omega} = 3A(12V) = 36W$$

$$P_{Tot} = 9A(12V) = 108W$$