

Name: _____

Key

Practice - 20.2 Ohm's Law: Resistance and Simple Circuits

1. The IR drop across a resistor means that there is a change in potential or voltage across the resistor. Is there any change in current as it passes through a resistor?

Explain.

No

$$I = \frac{V}{R}$$

The current depends upon V & R .
It is the voltage drop that drives the current.

2. What current flows through the bulb of a 3.00-V flashlight when its hot resistance is 3.60 Ω ?

$$I = \frac{V}{R} = \frac{3.00\text{V}}{3.60\ \Omega} = 0.833\text{A}$$

3. Calculate the effective resistance of a pocket calculator that has a 1.35-V battery and through which 0.200 mA flows.

$$I = \frac{V}{R} \Rightarrow R = \frac{V}{I} = \frac{1.35\text{V}}{0.200 \times 10^{-3}\text{A}} = 6.75 \times 10^3\ \Omega$$

4. What is the effective resistance of a car's starter motor when 150 A flows through it as the car battery applies 11.0 V to the motor?

$$I = \frac{V}{R} \Rightarrow R = \frac{V}{I} = \frac{11.0\text{V}}{150\text{A}} = 7.33 \times 10^{-2}\ \Omega$$

5. How many volts are supplied to operate an indicator light on a DVD player that has a resistance of 140 Ω , given that 25.0 mA passes through it?

$$V = IR = (25.0 \times 10^{-3}\text{A})(140\ \Omega) = 3.50\text{V}$$

6. A. Find the voltage drop in an extension cord having a $0.0600\text{-}\Omega$ resistance and through which 5.00 A is flowing.

$$V = IR = (5.00\text{ A})(0.0600\text{ }\Omega) = \boxed{0.300\text{ V}}$$

- B. A cheaper cord utilizes thinner wire and has a resistance of $0.300\text{ }\Omega$. What is the voltage drop in it when 5.00 A flows?

$$V = IR = (5.00\text{ A})(0.300\text{ }\Omega) = \boxed{1.50\text{ V}}$$

- C. Why is the voltage to whatever appliance is being used reduced by this amount?

The voltage is fixed coming out of the outlet. A voltage drop in the cord leaves less for the appliance.

7. A power transmission line is hung from metal towers with glass insulators having a resistance of $1.00 \times 10^9\text{ }\Omega$. What current flows through the insulator if the voltage is 200 kV ? (Some high-voltage lines are DC.)

$$I = \frac{V}{R} = \frac{200 \times 10^3\text{ V}}{1.00 \times 10^9\text{ }\Omega} = \boxed{2.00 \times 10^{-4}\text{ A}} \\ = 0.200\text{ mA}$$